

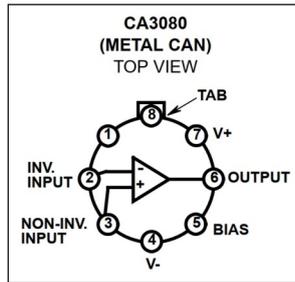
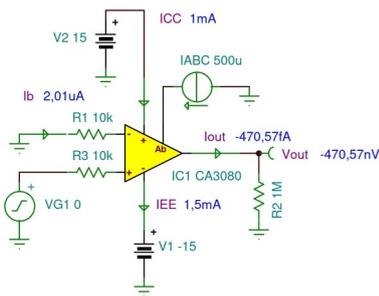


# CA3080 Operational Transconductance Amplifier Macro Model



## DC Characteristics

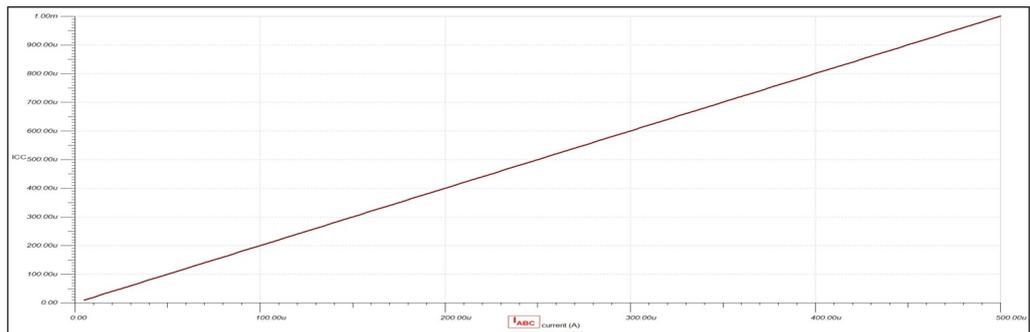


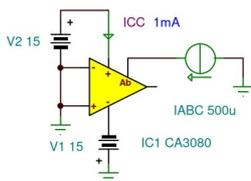
## Amplifier Supply Current vs Amplifier Bias Current


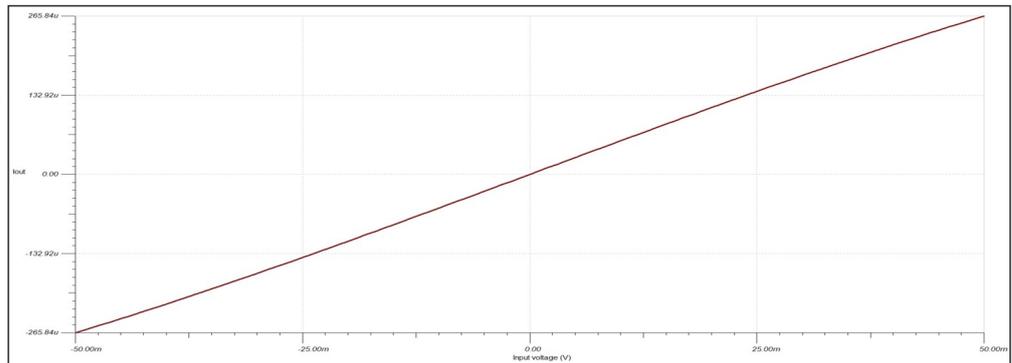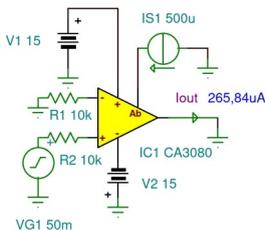
## Output Current vs Input Voltage ( $I_{ABC} = 500 \mu A$ )



## Amplitude Modulator

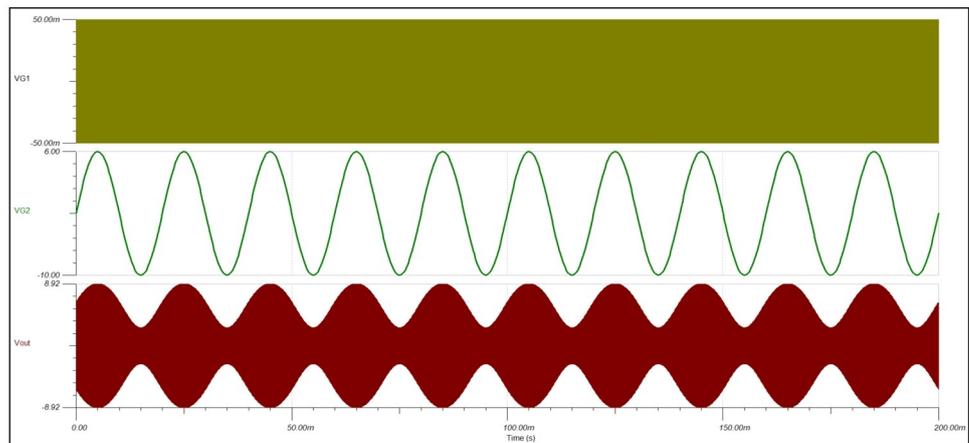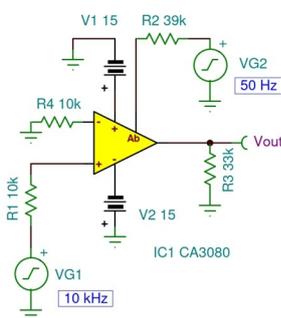

The modulator's linearity improves when the BIAS input is not driven by a voltage source with a series resistance. Superior performance is obtained by driving the BIAS node with a current source instead, for example by using the collector of a PNP transistor as the bias current source.