

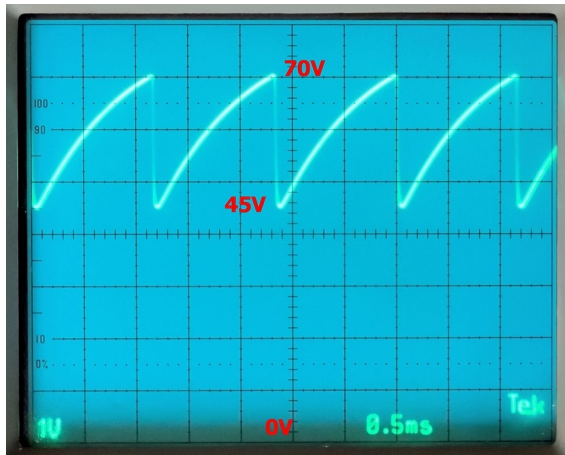
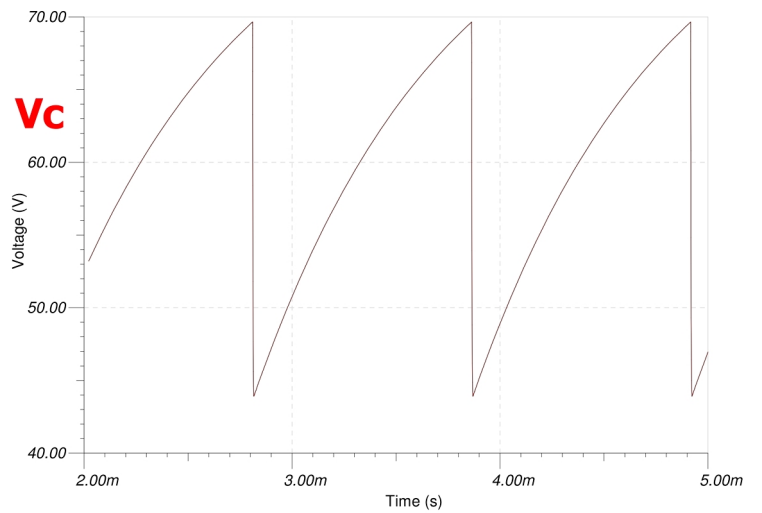
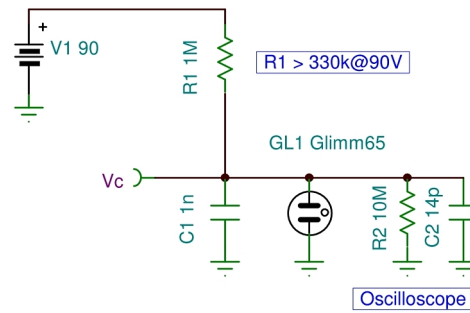
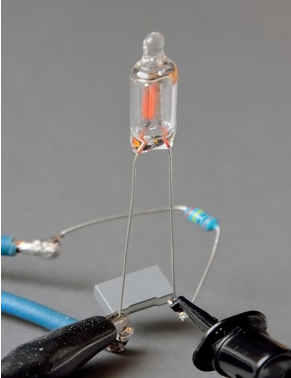
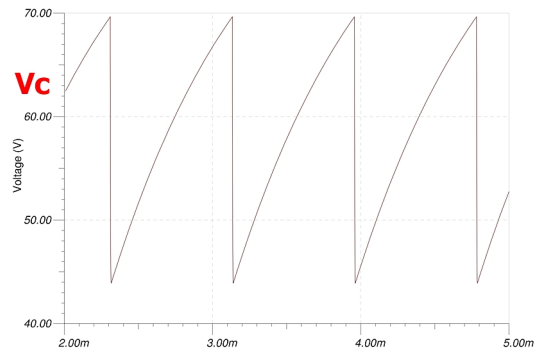


65V Neon Lamp Macro Model

Relaxation Oscillator:

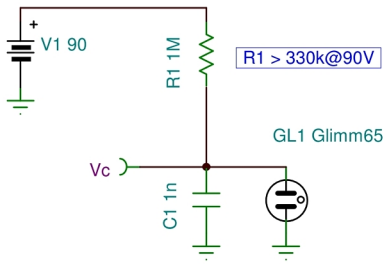

DC Transfer Characteristics:

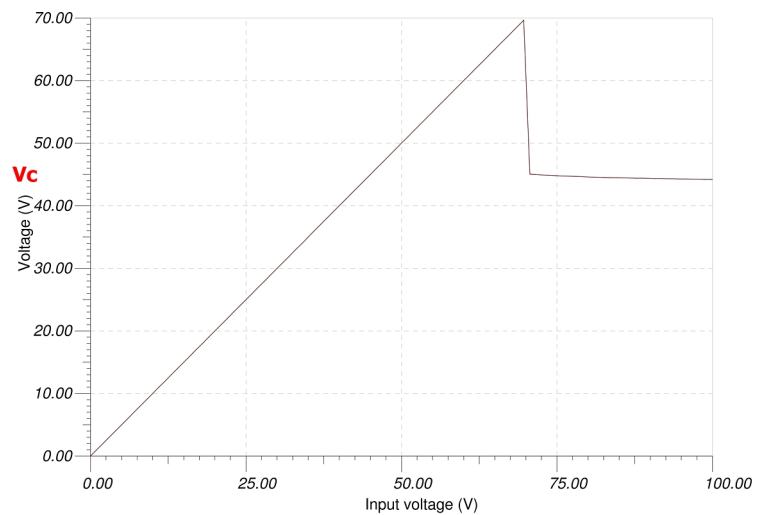

Neon Bulb Sine Wave Generator:

